NORTHBRIDGE TECHNICAL COLLEGE

EEN 120 Circuit Theory

Final examination - Academic year 2023, semester 1

Time allowed: 3 hours Total marks: 100 Lecturer: Eng. S. Mulenga

Instructions: answer ALL questions. Write clearly. Show all working.

Question 1: AC circuits

(a) Explain the key ideas of AC circuits with examples.

(b) Apply AC circuits to a practical problem of your choice.

Question 2: Ohm's law

(a) Explain the key ideas of Ohm's law with examples.

(b) Apply Ohm's law to a practical problem of your choice.

Question 3: Thevenin's theorem

(a) Explain the key ideas of Thevenin's theorem with examples.

(b) Apply Thevenin's theorem to a practical problem of your choice.